

## Online 1 (Boolean Algebra)

Subsection: C2

Duration: 25 minutes

### **Problem Description:**

Reduce the *((Last three Digits of StudentID - 1 ) % 6)th* Boolean function in the following list and implement the reduced circuit in Logisim using simple gates only. You must use the 7400-series IC chips: IC 74x04, IC 74x08, and IC 74x32 corresponding to the logic gates. Make sure to use **minimum no. of logic gates**. You must submit both the simplification steps and the circuit.

- 0)  $A + A'B'C + A'B'D + A'C'D'$
- 1)  $C'A'B + C'A'D + C'B'D' + C$
- 2)  $CAD' + CB'A' + CB'D + C'$
- 3)  $B'A'D' + B + B'C'A + B'C'D$
- 4)  $A' + ABD' + AC'B' + AC'D$
- 5)  $BA'C' + BA'D + B' + BCD'$

### **Submission:**

- 1. Create a folder using your roll number.
- 2. Put all your circuit files in the folder.
- 3. Put the PDF file containing your simplification steps in the folder. The simplification steps must be handwritten.
- 4. Create a zip file using your roll number and submit it.
- 5. If any kind of copying is detected, you will receive -100% marks.